

# CAD Programming Assignment 2

## Static Timing Analysis

(Due: 11/15)

### 1. Problem Description

Given a gate-level netlist and a cell library, find the longest and the shortest delay and their corresponding path under given input pattern.

**There are 3 steps to follow:**

- Step 1:** Build the delay graph according to the given netlist.
- Step 2:** Calculate the delay of each instance in the graph following topological order.
- Step 3:** Find the longest and the shortest delay and their corresponding path.

### 2. Input Format

#### (a) Flattened gate-level Verilog netlist (.v)

This file follows the standard Verilog gate-level syntax.

To simplify the problem, the given netlist is flattened, i.e., only one module exists in the file. Also, only three kinds of cells (NAND2, NOR2, INV) will appear in this file. Sequential circuits are not necessary to be considered.

Your program should be able to deal with extra space (or TAB), extra new lines, block comments (/\*\*/), and the comment lines starting with double slash (//) in this netlist file. Below is a simple example. Please note that the delay values in this example are just assumptions to simplify the calculation. Actual delay should be obtained from the given library information.

```
module prob2(n11, n12, n13, n1, n2, n3);
  output n11, n12, n13;
  input n1, n2, n3;
  //internal wires
  wire n4, n5, n6, n7, n8, n9, n10;
  INVX1 g1(.ZN(n4), .I(n1));
  INVX1 g2(.ZN(n5), .I(n2));
  NANDX1 g3(.ZN(n6), .A1(n4), .A2(n5));
  INVX1 g4(.ZN(n7), .I(n5));
  NOR2X1 g5(.ZN(n8), .A1(n4), .A2(n3));
  INVX1 g6(.ZN(n9), .I(n6));
  NOR2X1 g7(.ZN(n10), .A1(n6), .A2(n7));
  NANDX1 g8(.ZN(n11), .A1(n7), .A2(n8));
  NOR2X1 g9(.ZN(n12), .A1(n9), .A2(n10));
  NOR2X1 g10(.ZN(n13), .A1(n10), .A2(n8));
endmodule
```

 


Figure 1 : An example of the gate-level netlist and its corresponding description

### (b) Simplified liberty file (*test\_lib.lib*)

This file is simplified from the standard liberty format, which collects the timing and power information for each cell. The default units are also given in the file, which are ns (timing), pF (capacitance), V (voltage), and mA (current).

To simplify the problem, we assume that the timing and power information of the same output is the same for all input path, i.e., A1->ZN and A2->ZN have the same delay and power. Therefore, only one table is recorded for each output.

The table index is defined in *lu\_table\_template*, which include total output loading and input transition time. Please note that the total output loading and input transition time should be calculated based on the real circuit connection. The input capacitance of a cell is the output loading of the preceding cell. The output rising/falling time of a cell will be the input transition time of the succeeding cells.

Check "[LibertyFile.pdf](#)" for examples and more details. For simplicity, the numbers in the example may not be the same as in the given library file. TA will always use the same .lib file given to you to verify your program. We only utilize the timing information in HW2, power information will be used later in HW3.

## 3. Output Format

After executing your program, three output files should be generated for each step listed in the very beginning of this assignment. You should follow the naming rules as below.

For example, if the file name of the netlist file is "*example.v*", the <case\_name> would be "*example*".

Step 1: <student\_id>\_<case\_name>\_load.txt

Step 2: <student\_id>\_<case\_name>\_delay.txt

Step 3: <student\_id>\_<case\_name>\_path.txt

### (a) Step 1: Calculate output loading of each instance

Construct the circuit graph according to the given netlist. In this step, we proceed to verify the correctness of the graph construction by checking the output loading of each cell. The output loading of each cell would be the summation of the input capacitance of all the fanout cells. For the primary output in the given netlist, please set the output loading as 0.03pF.

Sort your results in descending order and name the file as "<student\_id>\_<case\_name>\_load.txt".

If the output loadings are identical, sort them according to instance number in ascending order.

Besides, you must print each value to the 6th decimal places.

```
g8 0.030000
g9 0.030000
g10 0.030000
.....
g4 0.017647
g1 0.017337
g6 0.010501
```

**(b) Step 2: Calculate propagation delay, and output transition time of each instance**

Before finding the worst-case delay path for the whole circuit, you must determine the propagation delay and output transition time of each instance based on the circuit connection. Input transition time is defined by the input that arrives latest if the instance has multiple inputs. Propagation delay and output transition time of the instance is then defined by the worst-case output, i.e., you need to calculate both output situations (output = 0 & 1), the one that has larger cell propagation delay will be the worst-case output.

If the output is 0, output transition time is defined by its output falling time.

If the output is 1, output transition time is defined by its output rising time.

To verify the results of this step, please report the worst-case output and timing information of each instance in the following format. Each row shows an instance name, worst-case output value, corresponding worst-case delay, and output transition time in order. Also, we assume that each wire between any two instances has 0.005ns delay.

Sort your results according to delay value in descending order and name the file as

"<student\_id>\_<case\_name>\_delay.txt". If the delay values are identical, sort them according to instance number in ascending order. Besides, you must print value of propagation delay and output transition time to the 6th decimal places.

```
g9 1 0.089355 0.145344 // output=1, propagation delay=0.089355, output rise time=0.145344
g10 1 0.089355 0.145344
g8 1 0.079914 0.128288
g7 1 0.066956 0.112308
.....
g6 0 0.041380 0.049434 // output=0, propagation delay=0.041380, output fall time=0.049434
g4 0 0.034014 0.047876
g2 0 0.022635 0.033406
g1 0 0.022268 0.031807
```

**(c) Step 3: Find the longest path and the shortest path**

According to the delay information, the longest and the shortest path is reported in different lines. To simplify the results, only nets' name are required to be reported, instances' name is not required. You must output the longest and the shortest delays and their corresponding delay path based on the given library file "*test\_lib.lib*". If the instance has multiple input signals that has same arrival time, you can output either one of them.

Name the output file as "<student\_id>\_<case\_name>\_path.txt". Also, you must print the value of the path delay to the 6th decimal places.

```
Longest delay = 0.246039, the path is: n2 -> n5 -> n6 -> n10 -> n12
Shortest delay = 0.160504, the path is: n1 -> n4 -> n8 -> n11
```

#### 4. Important Notice

- (a) The delay time of each instance can be determined by the input transition time (the output transition time of its driving cell) and the output loading (the total input capacitance for all fanout gates) according to the given delay table.

Boundary Conditions:

- Set input transition time of each primary input as **0ns**
- Set output loading of each primary output as **0.03pF**

- (b) To simplify the problem, there are several assumptions while calculating the worst-case delay as below.

- If there are multiple paths from cell inputs to cell output, input transition time is defined by the input that arrives later.
- For the propagation delay, there are two tables (`cell_rise`, `cell_fall`).  
If the output value of this cell is 1, use the table `cell_rise`.  
If the output value of this cell is 0, use the table `cell_fall`.
- For the output transition time, there are also two tables (`rise_transition`, `fall_transition`).  
If the output value of this cell is 1, use the table `rise_transition`.  
If the output value of this cell is 0, use the table `fall_transition`.  
The successor cells will use this value as the input transition time.
- For wire delay, assume every wire between any two instances has **0.005ns** delay.

- (c) Print all value to the 6th decimal places except the worst-case output value of each instance.

#### 5. Compile and Execution

- You must include "***Makefile***" for TA to compile your code.
- Name of the execution file after compiling must be "***<student\_id>***"
- Your program must be able to receive commands in following format.

```
./<student_id> netlist_file -l test_lib.lib
```

For example:

```
./311510369 example.v -l test_lib.lib
```

- Be sure that it can compile and execute successfully on our workstation.
- Do not print any words on terminal when executing.

## 6. Grading Policy

### (a) Correctness (80%)

You are encouraged to complete this assignment step by step. For each testcase, you would get your grade for each step with corresponding percentage of the total grade as shown below.

- Step 1 result (30%)
- Step 2 result (30%)
- Step 3 result (20%)

### (b) Runtime performance (20%)

The remaining 20% not included for the correctness of each step would be rated by the ranking of runtime among all students who pass all three steps. The ranking of runtime is based on the sum of execution time for each case. Please note that you would not get any grade for the runtime performance unless you pass all three steps.

For each case, the **runtime limit is 300 seconds**. It will be regarded as failed if you exceed the limitation. (Hint: Make good use of container of C++ STL to avoid exceeding runtime limit)

- \* Hidden cases will be used to evaluate your program.
- \* Violates file naming rules: -10 points
- \* Doesn't follow the requirements of output format: -20 points
- \* Print words on terminal while executing: -20 points
- \* **Plagiarism: -100 points**

## 7. Submission Steps

### (a) Put these files in a folder, the name of the folder is your student\_id.

- Source code(.cpp, .h), no naming restrictions for source code
- Makefile
- A simple report that explains the implementation details, name the report as "**<student\_id>\_report.pdf**"

### (b) Use the command below to compress the folder in linux environment, the compressed file name should also be your student\_id.

```
$tar cvf <student_id>.tar <student_id>
```

### (c) **Submit <student\_id>.tar to E3 before the deadline (11/15).**

- \* If you have any question, please ask on HW2 discussion forum of E3.